

**Class: XII**  
**Subject: Physics**  
**Topic: Current Electricity**  
**No. of Questions: 20**  
**Duration: 60 Min**  
**Maximum Marks: 60**

1. SQUID is a device used to
  - A. measure magnetic field changes with precision
  - B. measure electric field changes with precision
  - C. measure superconductivity
  - D. measure photo conductivity

Ans A

2. The dimensions of voltage (pd or emf) is
  - A.  $ML^2 T^{-3} I^{-2}$
  - B.  $ML^2 T^{-3} I^{-1}$
  - C.  $ML^2 T^3 I$
  - D.  $ML^2 T^{-2} I^{-1}$

Ans. B

Solution:

$$[V] = \frac{[W]}{[Q]} = \frac{ML^2 T^{-2}}{IT} = ML^2 T^{-3} I^{-1}.$$

3. Heating coil must have
  - A. high melting point & high resistance
  - B. high melting point & low resistance
  - C. low melting point & low resistance
  - D. low melting point & high resistance

Ans. A

4. A 20 W, 120 V light bulb and a 60 W, 120 V light bulb are connected in series across a 240V line. Assuming that the resistance of each bulb does not vary with current, the current through the bulbs is
- A. 1 A
  - B.  $\frac{1}{3}$  A
  - C.  $\frac{1}{4}$  A
  - D. None

Ans. C

Solution:

$$\text{Resistance of I bulb} = \frac{(120)^2}{20} = 720\Omega$$

$$\text{Resistance of II bulb} = \frac{(120)^2}{60} = 240\Omega$$

$$\text{Current through the bulb} = \frac{240}{720 + 240} = \frac{240}{960} = \frac{1}{4} \text{ A}$$

5. Carbon resistors used in electronic circuits are marked for their resistance value and tolerance by a colour scheme. A given resistor has a color scheme brown, black, blue and gold. Its value in ohm is
- A.  $1.0 \times 10^3 \pm 5\%$
  - B.  $3.2 \times 10^5 \pm 5\%$
  - C.  $1.0 \times 10^6 \pm 10\%$
  - D.  $10 \times 10^6 \pm 5\%$

Ans. D

Solution:

Brown - black - blue & gold  
 $10 \times 10^6 \pm 5\%$

6. A resistor is in the left gap and a (NTC) semiconductor is in the right of a meterbridge. Balancing length is noted (l) Both are heated so that change of resistance in them is the same. Now balancing length is
- A. equal to
  - B. greater than
  - C. less than
  - D. depends on temperature change


Ans. B

Solution:

Resistance of resistor in the left gap increases. Resistance of NTC in the right gap

decreases. Balancing length adjacent to resistor increases. Thus balancing point shifts to right. So it is greater than  $l$

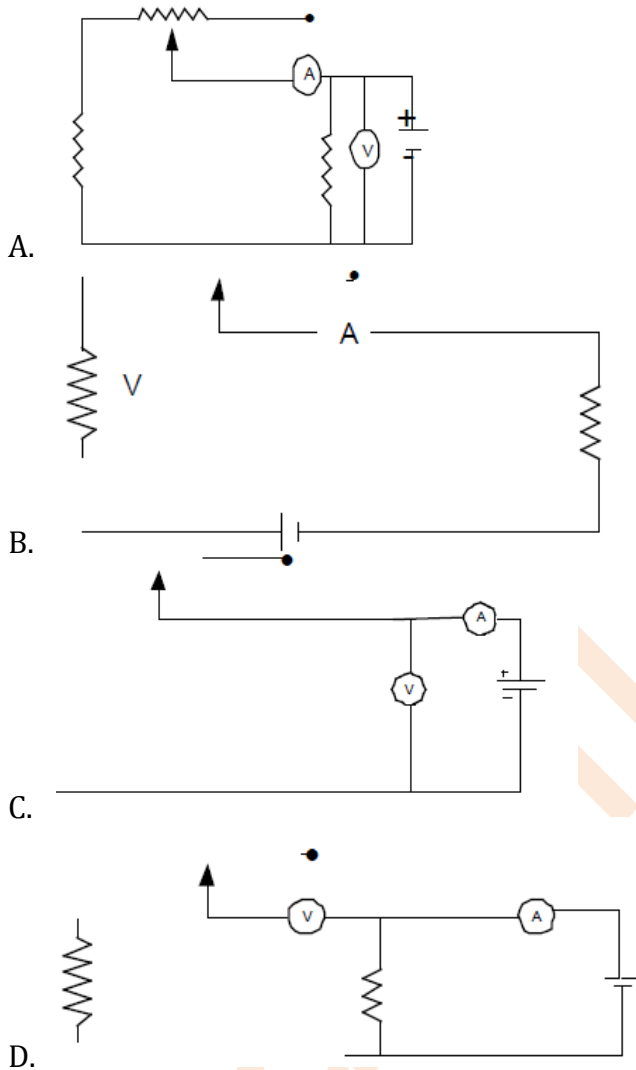
7. Which of the following circuit is correct for the verification of ohm's law?



Ans. A

To verify Ohm's law, ammeter is connected in series and voltmeter is connected in parallel with one of the resistance which is varied by changing the resistance.

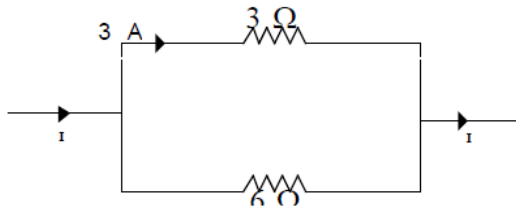8. Calculate the current  $I$  in the circuit shown



- A. 9A
- B. 4.5A
- C. 3A
- D. 1.5A

Ans. B

Solution:

$$\text{Current in one branch} = \frac{\text{Main current} \times \text{Resistance of other branch}}{\text{sum of resistance s}}$$

$$3 \times \frac{I \times 6}{9} \Rightarrow I = \frac{27}{6} = 4.5A$$

9. Four resistances 15, 12, 4 & 10  $\Omega$  are connected in cyclic order to form wheatstone network. The resistance to be connected in,parallel with 10  $\Omega$  to balance the network is
- A. 5  $\Omega$
  - B. 10  $\Omega$
  - C. 8  $\Omega$
  - D. 20  $\Omega$

Ans. B

Solution:

X is the resistance connected in parallel with 10  $\Omega$

$$\frac{P}{Q} = \frac{R_p}{S} \quad \frac{15}{12} = \frac{R_p}{4} \quad R_p = \frac{15 \times 4}{12} = 5$$

$$\frac{10x}{10+x} = 5 \quad 10x = 50 + 5x \quad x = 10\Omega$$

10. An example of a non-ohmic device is
- A. potentiometer wire
  - B. platinum resistance thermometer
  - C. thermistor
  - D. copper wire

Ans. C

11. A platinum wire has a resistance of  $10 \Omega$  at  $0^\circ\text{C}$  and  $20 \Omega$  at  $273^\circ\text{C}$ . Then the value of temperature coefficient of platinum is

- A.  $273^\circ\text{C}$   
 B.  $\left(\frac{1}{273}\right)^\circ\text{C}$   
 C.  $\left(\frac{1}{273}\right)^\circ\text{C}^{-1}$   
 D.  $(273) \text{K}^{-1}$

Ans. C

Solution:

$$\alpha = \frac{R - R_0}{R_0 \theta} = \frac{10}{10 \times 273} = \left(\frac{1}{273}\right)^\circ\text{C}^{-1}$$

12. The resistance of 10 m potentiometer wire is  $20 \Omega$ . A resistance box is connected in series with a cell of emf 2 V & internal resistance  $1\Omega$  to the ends of potentiometer wire. The value of resistance to be unplugged in resistance box so that there is a fall of potential 0.01 mV/cm

- A.  $1979 \Omega$   
 B.  $2979 \Omega$   
 C.  $4000 \Omega$   
 D.  $3979 \Omega$

Ans.D

Solution:

R be resistance of potentiometer wire & R' to be resistance unplugged;

Fall of potential across potentiometer wire


$$= \text{Current} \times \text{resistance of potentiometer wire} = \frac{E}{R + R' + r} \times R.$$

$$\text{Fall of potential / cm} = \frac{1}{1000} \left[ \frac{ER}{R + R' + r} \right]$$

$$0.01 \times 10^{-3} = \frac{1}{1000} \left[ \frac{2 \times 20}{20 + R' + 1} \right] 0.01 = \frac{40}{21 + R'}$$

$$21 + R' = 4000 \quad R' = 3979 \Omega$$

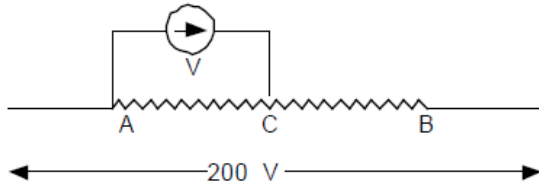
13. AB is a uniform wire of resistance 2000 ohm and C is the midpoint of AB. A voltmeter of resistance 1000 ohm is connected between A and C. Then the reading of the voltmeter, when the P.D. applied across AB is 200 V is



- A. 66.6 V
- B. 33.3 V
- C. 133.2 V
- D. 200 V

Ans.A

Solution:

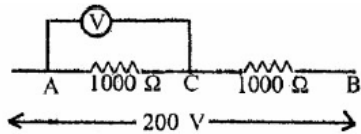

$$I = \frac{\text{Total emf}}{\text{Total resistance}} = \frac{200}{R_p + 1000}$$

$$= \frac{200}{1500} = 2/15 A$$


$$\text{Voltmeter reading } V = I \times R_{\text{eff}}$$

$$= \frac{2}{15} \times 500 = \frac{200}{3} = 66.6 V$$

14. A carbon composition resistor has the following colour code: Green, Blue, Yellow, Silver. Its resistance is
- A.  $560 \pm 56 \text{ k}\Omega$
  - B.  $560 \pm 28 \text{ k}\Omega$
  - C.  $56 \times 10^5 5.6 \text{ }\Omega$
  - D.  $5.6 \pm 2.8 \text{ k}\Omega$

Ans,A

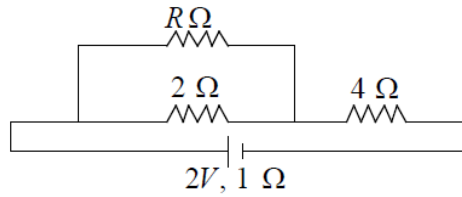15. A current of  $1/3 \text{ A}$  flows in the main circuit. Now, the resistance  $R$  is disconnected and then connected across the  $4 \text{ }\Omega$  resistance. The current in the circuit now is



- A.  $\frac{1}{2}$  A
- B. 4 A
- C.  $\frac{2}{9}$  A
- D.  $\frac{6}{13}$  A

Ans. D

Solution:

$$\text{Current } I = \frac{\text{Total emf}}{\text{Total resistance}}$$

$$\frac{1}{3} = \frac{2}{\frac{2R}{R+2} + 4 + 1} \Rightarrow 6 = \frac{2R}{R+2} + 5 \Rightarrow 2R = R + 2 \Rightarrow R = 2\Omega$$

∴ When  $R = 2\Omega$  is connected across 4 Ω

$$I = \frac{2}{2 + 1 + \frac{4 \times R}{4 + R}} = \frac{2}{3 + \frac{8}{6}} = 6/13 \text{ A}$$

16. Consider 6 branches of 10 identical cells connected in series the emf and the internal resistance of each cell being 1.5 volts and 1 ohm respectively. If the group of cells sends a current I through an external resistance of 20 ohms, then the value of this current (in amperes) in

- A. 0.25
- B. 0.14
- C. 0.70
- D. 0.85


Ans. C

Solution:

$$I = \frac{mnE}{mR + nr} = \frac{6 \times 10 \times 1.5}{6 \times 20 + 10 \times 1} = \frac{90}{130} = 0.69A = 0.70A$$

17. A Wire of length 40 cm of resistance  $0.1 \Omega/\text{cm}$  is bent into the form of a circle. A cell of emf 2 V and negligible internal resistance is connected across 2 diagonally opposite points. The current in each branch is
- A. 3A
  - B. 2A
  - C. 1A
  - D. 4A

Ans.

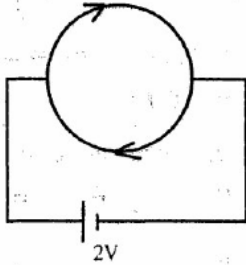

Resistance of each branch =  $20 \times 0.1 = 2\Omega$

$$\text{Total current} = \frac{2}{R_{\text{eff}}} = \frac{2}{1} = 2A$$

$$\therefore \text{Current in each branch} = \frac{2}{2} = 1A$$

18. Two resistors  $400 \Omega$  and  $800 \Omega$  are connected in series with a 6 V battery. An ammeter of  $10 \Omega$  resistance connected in series in the circuit reads
- A. 5.96 A
  - B. 6.96 A
  - C. 4.96 mA
  - D. 10 mA


Ans.C

Solution:

$$I = \frac{V}{R} = \frac{6}{800 + 400 + 10} = \frac{6}{1210} = 4.96mA$$



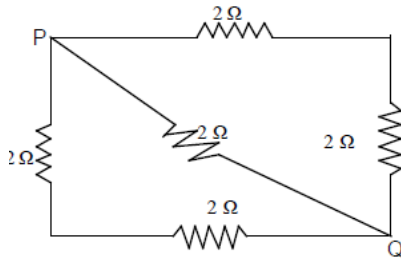
19. The resistance between P and Q in the figure shown is



- A.  $1 \Omega$
- B.  $3/2 \Omega$
- C.  $6 \Omega$
- D.  $4 \Omega$

Ans. A

Solution:

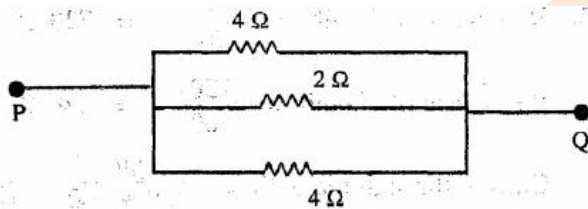

$$\frac{1}{R_p} = \frac{1}{4} + \frac{1}{2} + \frac{1}{4}$$

$$\frac{1}{R_p} = \frac{1+2+1}{4} = 1\Omega$$

$$\therefore R_p = 1\Omega$$

20. Good resistance coils are made of

- A. Gold
- B. Silver
- C. Copper
- D. Manganin

Ans. D

Fact