

Class: XII
Subject: Physics
Topic: Electronic Devices
No. of Questions: 20
Duration: 60 Min
Maximum Marks: 60

1. p-n junction has a thickness of the order of
- 1 cm
 - 1 mm
 - 10^{-6} cm
 - 10^{-12} cm

Ans. C

Solution:

A p-n junction has a thickness of order of 10^{-6} cm.

2. Which of the following are not electromagnetic waves?
- cosmic rays
 - gamma rays
 - β -rays
 - X-rays

Ans. C

Solution:

β - rays are not electromagnetic waves

3. The question contains statement-1 (Assertion) and Statement-2 (Reason).
The question has four choices. You have to select the correct choice.
Assertion: NAND or NOR gates are called digital building blocks.

Reason: The repeated use of NAND (or NOR) gates can produce all the basic or complicated gates.

- If statement-1 is true but statement-2 is false
- If statement-1 is false and statement-2 is true.


- c. If both statement-1 and statement-2 are true and statement-2 is the correct explanation of statement-1
- d. If both statement-1 and statement-2 are true but statement-2 is not the correct explanation of statement-1

Ans. C

Solution:

These gates are called digital building blocks because using these gates only (either NAND or NOR) we can compile all other gates also (like OR, AND, NOT, XOR).

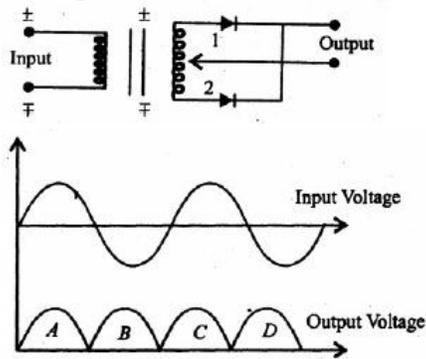4. A full wave rectifier circuit along with the input and output voltages is shown in the fig.



The contribution to output voltage from diode - 2 is

- a. A, C
- b. B, D
- c. B, C
- d. A, D

Ans. B

Solution:

As stated.

5. The reverse bias in a junction diode is charged from 5 V to 15 V the value of current changed from 38 μ A to 88 μ A. The reverse resistance of junction diode will be
- a. $4 \times 10^5 \Omega$
 - b. $3 \times 10^5 \Omega$
 - c. $2 \times 10^5 \Omega$

d. $10^6 \Omega$

Ans. C

$$\text{Reverse resistance} = \frac{\Delta V}{\Delta I} = \frac{(15 - 5)}{(88 - 38) \times 10^{-6}} = 2 \times 10^5 \Omega$$

6. What configuration of transistor is used for amplifying the voltage?

- a. CE
- b. CB
- c. CC
- d. None of the above

Ans. A

7. What is the Boolean equation for the logic gate shown?



- a. $Y = A + \bar{B}$
- b. $Y = \bar{A} + \bar{B}$
- c. $Y = \bar{A} + B$
- d. $Y = \bar{A} + \bar{B}$

Ans. C

Solution:

As stated.

8. An intrinsic semiconductor at absolute zero of temperature behaves as

- a. an insulator
- b. a metallic conductor
- c. a superconductor
- d. a semiconductor

Ans. A

Solution;

The phenomenon of spontaneous electron-hole pair generation is about at 0 K.

9. Read the statement carefully

- x: the resistivity of a semiconductor can be decreased by adding suitable impurity to it.
- Y: introduction of impurity to semiconductor creates excess charge carriers of one type.

Z: introduction of small quantity of the order 1 part per 10⁶, controls the conductivity in the predictable manner.

Select the correct statement(s) from the following:

- a. both X and Y are true and Z is false
- b. both X and Y are true and Z is the correct reason for X
- c. both X and Y are true and Y is the correct reason for X
- d. X, Y and Z are true and Z is the correct reason for X

Ans. C

Solution;

As stated.

10. The following truth Table

A	B	Y
0	0	1
1	0	0
0	1	0
1	1	0

is for

- a. OR gate
- b. AND gate
- c. NOT gate
- d. NOR gate

Ans. D

Solution:

d)

A	B	OR gate	NOR
0	0	0	1
1	0	1	0
0	1	1	0
1	1	1	0

Y corresponds to a NOR gate.

11. To a germanium sample, traces of gallium are added as an impurity. The resultant sample would behave like

- a. a conductor
- b. a p-type semiconductor
- c. an n-type semiconductor
- d. an insulator

Ans. B

Solution:

As Ga belongs to group IIIA it will form a p-type semiconductor.

12. The typical ionization energy of a donor in silicon is


- a. 1.0 eV
- b. 0.1 eV
- c. 0.01 eV
- d. 0.001 eV

Ans. A

Solution:

Ionization energy of donor silicon = 1.0 eV.

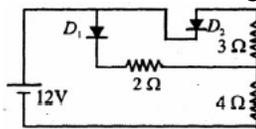13. In the circuit of figure treat the diodes as ideal. Current in the 4 ohm resistor is



- a. 2 A
- b. 3 A
- c. $12/7$ A
- d. $30/13$ A

Ans. A

Solution;

D_1 is forward biased and D_2 is reverse biased.

So, no current will flow from D_2 or 3Ω .

The $R_{\text{eff}} = 2\Omega + 4\Omega = 6\Omega$

$$I_{4\Omega} = \frac{12\text{ V}}{6\Omega} = 2\text{ A.}$$

14. What is depletion region?

- a. Region where there are less charges
- b. Region where there are less of positive charges
- c. Region where charges move and forms an insulating region
- d. None of the above

Ans. D

15. Read the passage and Answer the question below:

In a p-n junction, the current I can be expressed as

$$I = I_0 \left(e^{\frac{eV}{kT}} - 1 \right)$$

Where I_0 is called the reverse saturation current, V the voltage across the diode and is positive for forward bias and negative for reverse bias and I is the current through the diode, k is the Boltzmann's constant ($8.6 \times 10^{-5} \text{eVK}^{-1}$) and T is the absolute temperature. If for a diode, $I_0 = 5 \times 10^{-12} \text{A}$ and $T = 300 \text{K}$, then

What is the dynamic resistance?

- a. 0.0337Ω
- b. 1.0223Ω
- c. 4.0556Ω
- d. 1.0042Ω

Ans. A

Solution:

Now, $I = 2.9643 \text{A}$;

$$\Delta V = 0.7 - 0.6 = 0.1 \text{V}$$

Therefore, dynamic resistance

$$= \frac{\Delta V}{\Delta I} = \frac{0.1}{2.9643} = 0.0337 \Omega$$